



Faculty of Engineering

AIN SHAMS UNIVERSITY

Third year mechatronics engineering

Computer Organization


Third part of the project

Represented by:

Shrouk Magdy Ibrahim	sec: 1
Salma Hussien Sayed	sec: 1
Abd-El-Rahman Mohamed Abd-El-Fattah	sec: 2
Abd-Allah Osama Korany	sec:2
Abd-El-Rahman Ahmed Abbas	sec:2


The executed program

Location	Instruction	Ac	Pc	IR
000	CLA	0000	001	7800
001	ADD 006	C1A5	002	1006
002	BUN 004	C1A5	004	4004
003	HLT	8184	004	7001
004	AND 007	8184	005	0007
005	BUN 003	8184	003	4003
006	C1A5			
007	93C6			

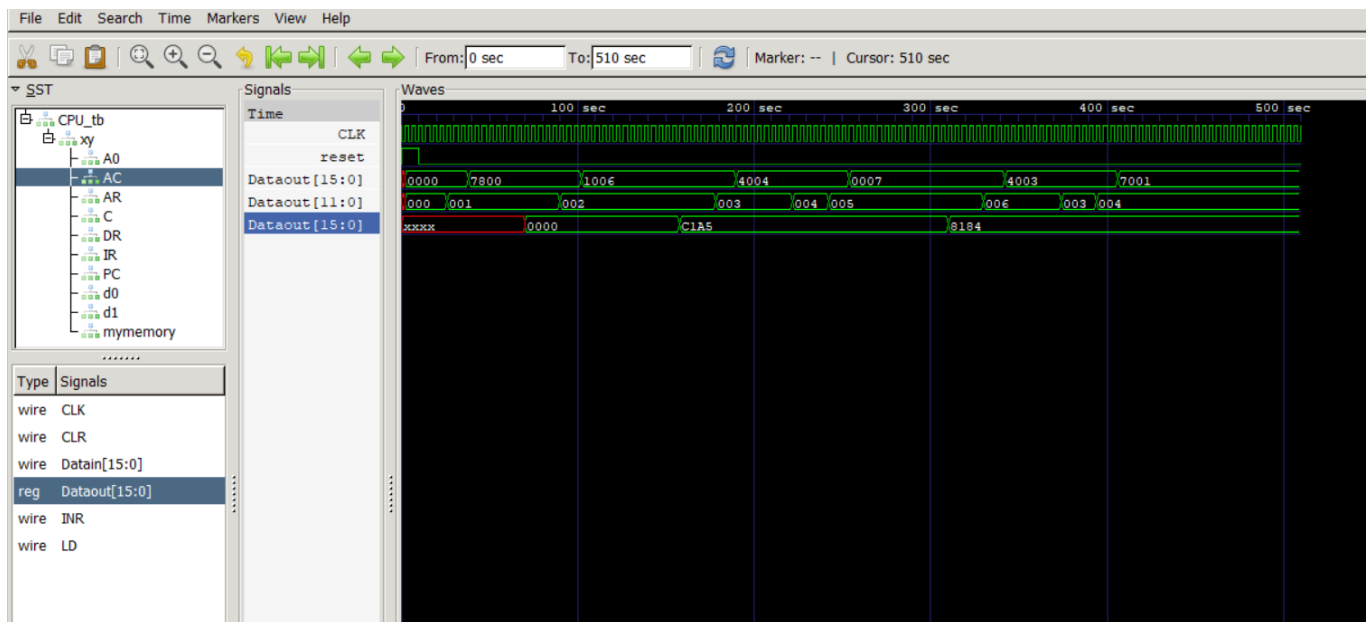

Design hints:

 1. The top level module will have:
 - a. Two inputs only: a *clock* and a global *reset* signal
 - b. One output: the accumulator *AC*




4. The memory module should have a sample test program for the CPU. Therefore, initialize the memory contents in your design with a small program.
5. For simplicity, let the first instruction in your program be at address 0.

```
module memory16(address,datain,dataout,R,W,CLK);
input CLK;
input R;
input W;
input [11:0]address;
input [15:0]datain;
output [15:0]dataout;
wire CLK;
wire R;
wire W;
wire [11:0]address;
wire [15:0]datain;
reg [15:0]dataout;
reg [15:0]memory16[0:4095];
initial
begin
memory16[0]=16'h7800;
memory16[1]=16'h1006;
memory16[2]=16'h4004;
memory16[3]=16'h7001;
memory16[4]=16'h0007;
memory16[5]=16'h4003;
memory16[6]=16'hC1A5;
memory16[7]=16'h93C6;
end
always@(posedge CLK)
begin
if (W==1)begin
memory16 [address]=datain;
end
else if (R==1)begin
dataout=memory16 [address];
end
end
endmodule
```


```
mem[0]=7800
mem[1]=1006
mem[2]=4004
mem[3]=7001
mem[4]=0007
mem[5]=4003
mem[6]=c1a5
mem[7]=93c6
```

-


Module CPU

 


Module Sequencer

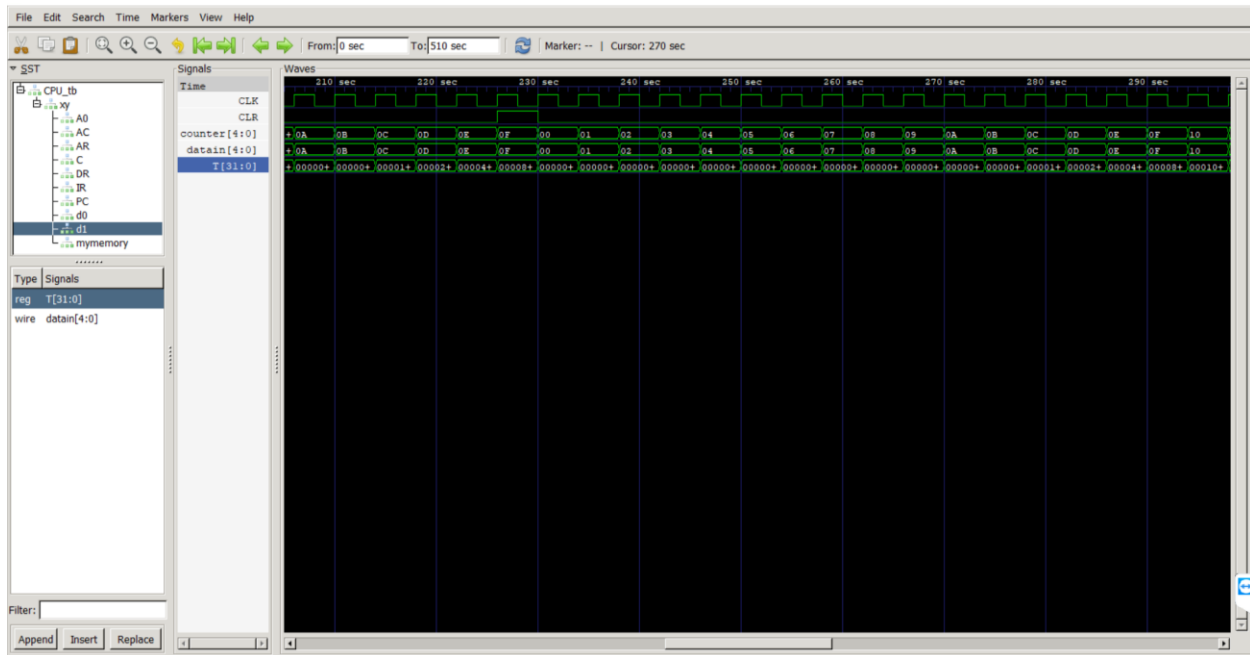


Module PC

 


Module AR

 


Module memory

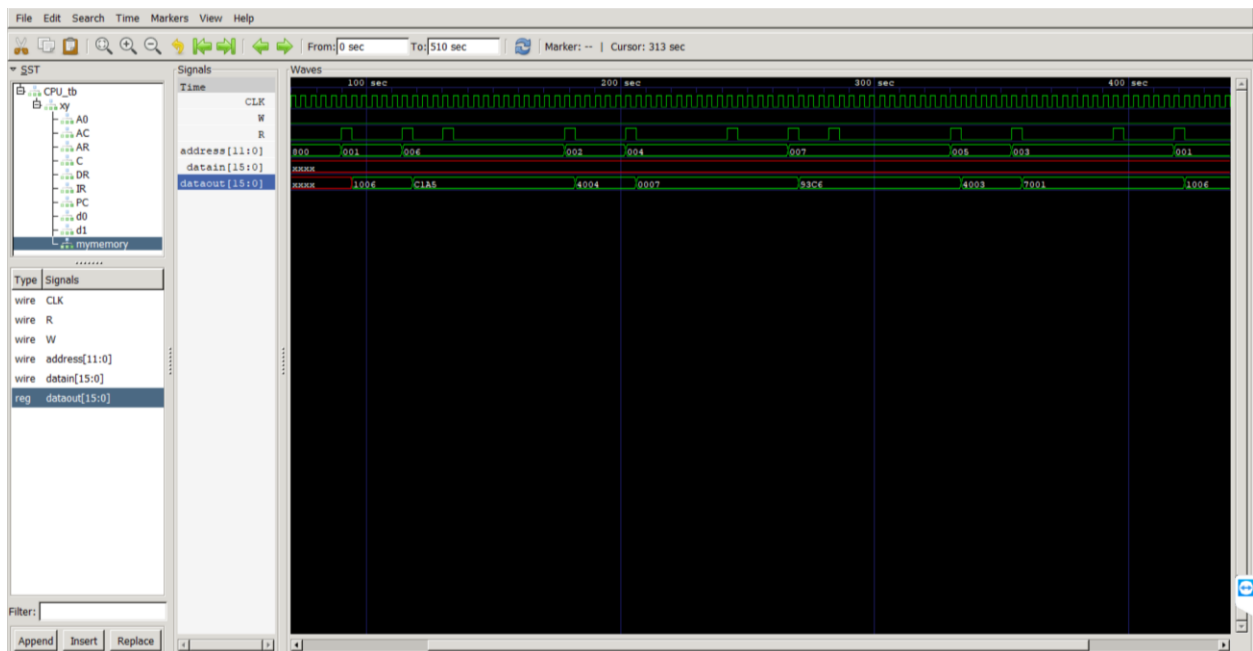


Module IR

 


Module decoder (for opcode)

 

Module DR

 

Module Alu

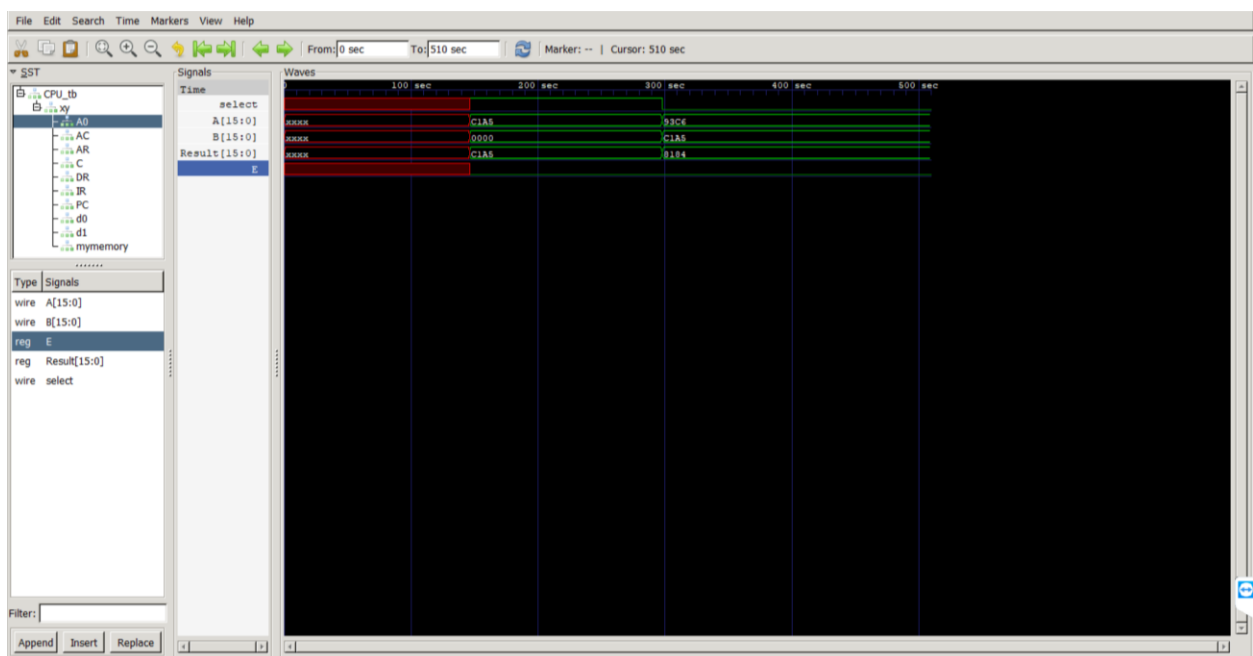

Module AC

