



Faculty of Engineering

AIN SHAMS UNIVERSITY

Third year mechatronics engineering

Computer Organization


Third part of the project

The implementation details of the design

Represented by:


Shrouk Magdy Ibrahim	sec: 1
Salma Hussien Sayed	sec: 1
Abd-El-Rahman Mohamed Abd-El-Fattah	sec: 2
Abd-Allah Osama Korany	sec:2
Abd-El-Rahman Ahmed Abbas	sec:2

The sequence of the code

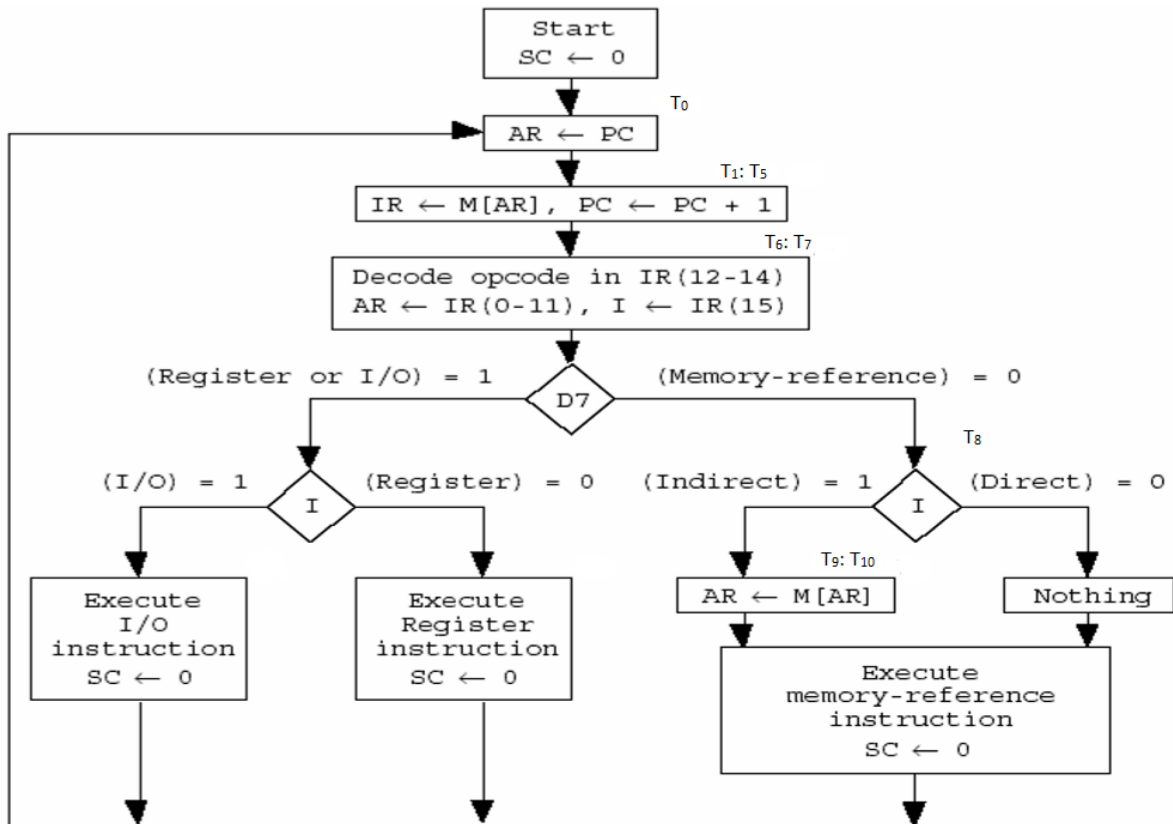

The diagram above shows the program sequence in CPU from fetching the instruction , decoding it and getting the effective address

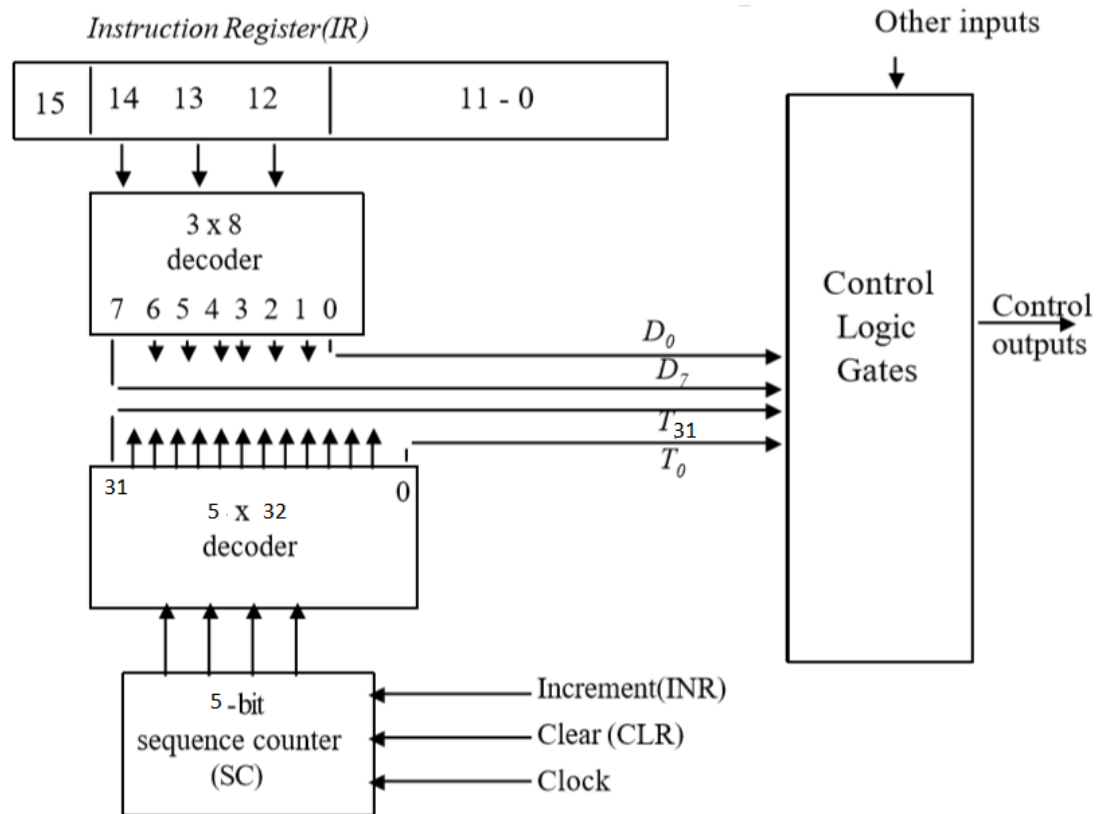
The sequencer & decoder (for opcode) modules



The sequencer module function is to organize the timing of the microoperations of the CPU from fetching ,decoding and execution.

The decoder module (for opcode) is used to determine which instruction is given from memory , register or input output instruction to instruction register.

The path of the data in CPU

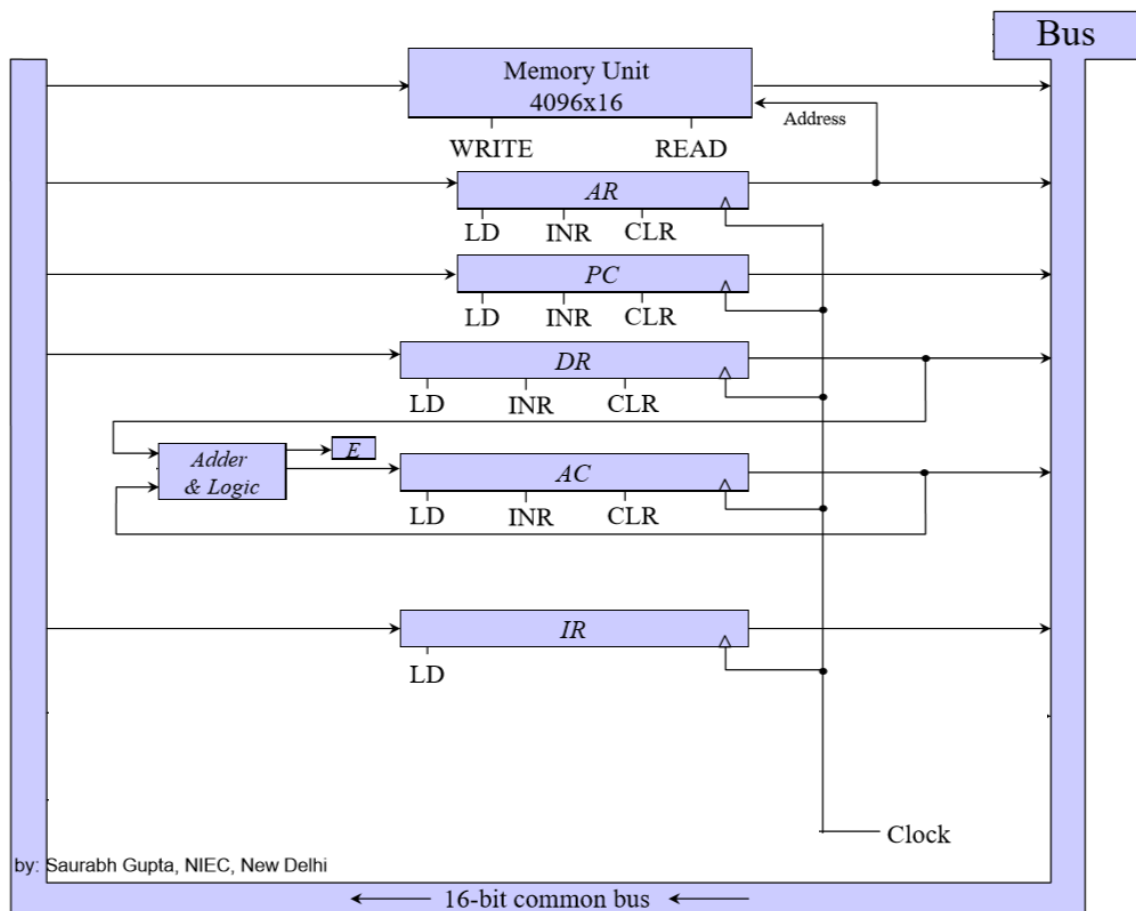


The diagram above shows the path of data in CPU between registers ,ALU and memory .It starts as address move from PC to AR to memory address then memory get the instruction to IR then from IR to AR , opcode and I-bit to determine type of instruction

*if it is memory instruction , we get the effective address of operand to execute the instruction, the output passes from ALU(if it is and or add only) to DR and finally to AC

*if it is register instruction , the instruction executed depends on the least significant bits [0:11]

The AR module

 

The AC module

